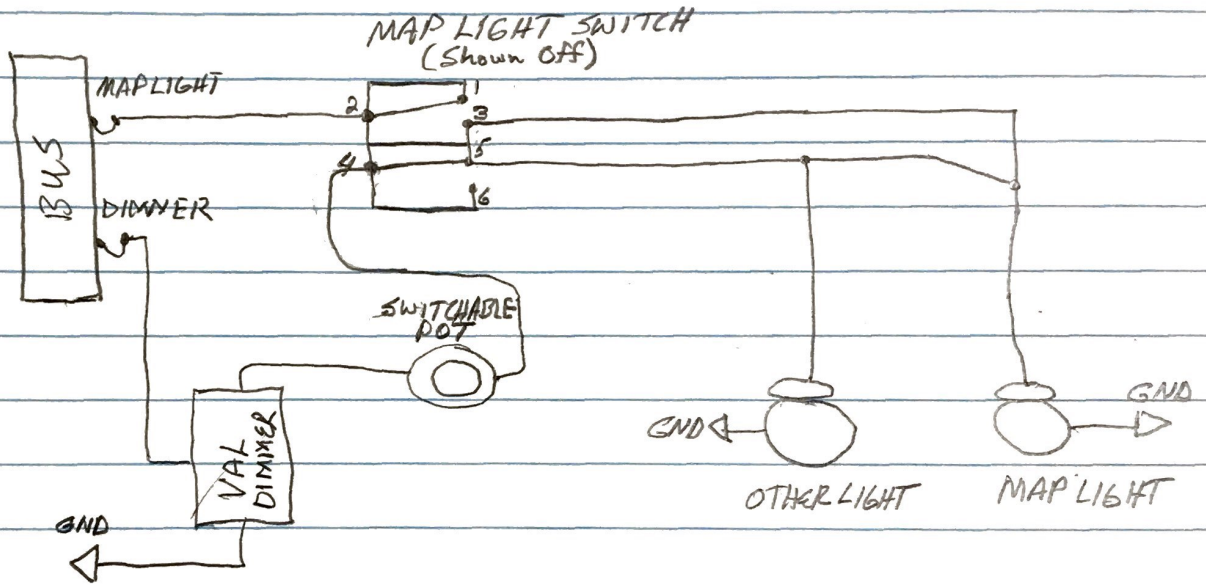


Map Light + Dimmable Light Set Circuit



- When MAP LIGHT switch is off, SWITCHABLE POT controls both lights w/ dimmer.
- When MAP LIGHT switch is on, DIMMER doesn't reach either light, but MAP LIGHT is on full bright.

MAP LIGHT SWITCH	SWITCHABLE POT	RESULT
OFF	OFF	No Light
ON	OFF	Full Bright Map Light
OFF	ON	Both lights controlled by DIMMER POT
ON	ON	Full Bright Map Light