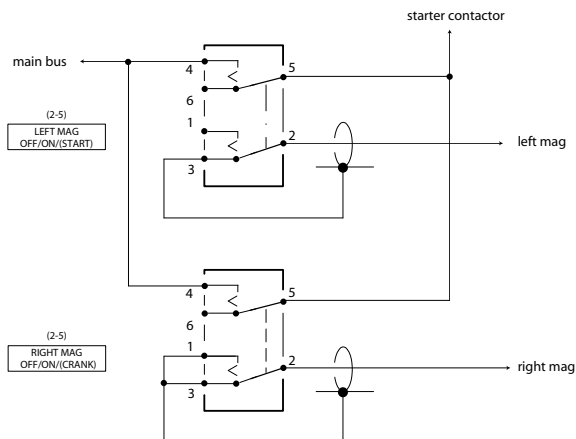


1) both mags off (engine killed)

both switches down


starter circuit:	off
left mag:	off
right mag:	off



2) crank with both mags off (no start)

left switch down, right up


starter circuit:	on
left mag:	off
right mag:	off

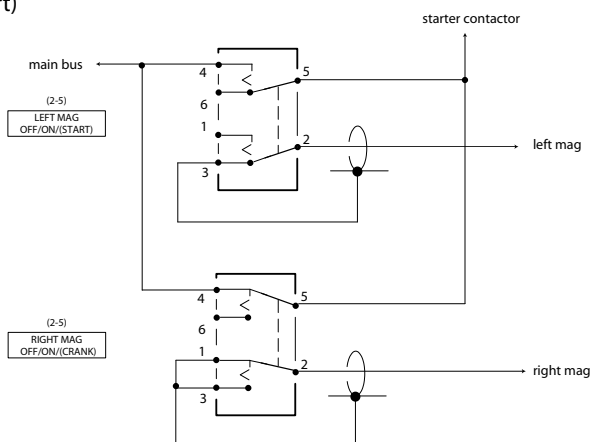

3) start with both mags hot

left switch up, right center

starter circuit:	on
left mag:	on
right mag:	on

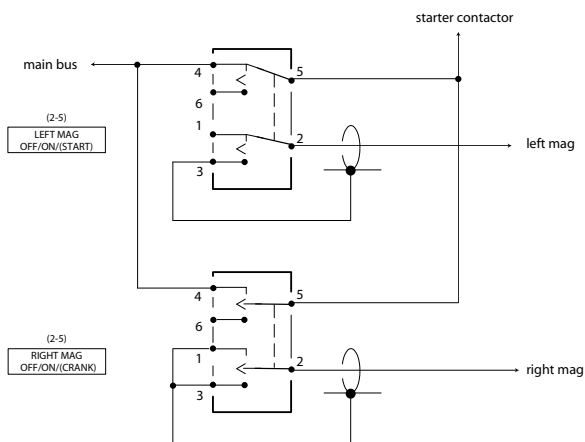

4) both mags on (engine running)

both switches center

starter circuit:	off
left mag:	on
right mag:	on

