



Now that the contactor coil is energized, it will hold and stay energized even if the ground power is unplugged. Current flows from the aircraft battery (unless it is completely dead) through the already closed ground power contactor contacts, through the coil and switch and diode and 2 amp circuit breaker to ground. The ground power switch should be shut off whenever the ground power is disconnected.